

Student Names: Elif Güler, Samed Düzçay  
Student IDs: 2015400099, 2015400027  
Group ID: 5

## Experiment 4 (Analysis of a Sequential Circuit)

### Preliminary Work:

**Step 1: State the inputs and outputs of the state registers.**

Inputs: N2, N1, N0

Outputs: S2, S1, S0

**Step 2: State the inputs and outputs of the combinational block.**

Inputs: S2, S1, S0, X

Outputs: N2, N1, N0, Y1, Y0

**Step 3: Write each output (including next state bits) as a function of the inputs.**

$$N2 = X((S2(S1+S0)') + S2'S1S0)$$

$$N1 = (S2'X)(S1^{\wedge}S0)$$

$$N0 = ((S2'X') + ((S1+S0)'(S2X')) + (S1X(S2+S0)')$$

$$Y1 = X'((S2(S1+S0)') + (S2'S1S0))$$

$$Y0 = (S2^{\wedge}S1)(S0+X)'$$


**Step 4: Draw the truth table for the combinational circuit.**

#	S2	S1	S0	X	N2	N1	N0	Y1	Y0
0	0	0	0	0	0	0	1	0	0
1	0	0	0	1	0	0	0	0	0
2	0	0	1	0	0	0	1	0	0
3	0	0	1	1	0	1	0	0	0
4	0	1	0	0	0	0	1	0	1
5	0	1	0	1	0	1	1	0	0
6	0	1	1	0	0	0	1	1	0
7	0	1	1	1	1	0	0	0	0
8	1	0	0	0	0	0	1	1	1
9	1	0	0	1	1	0	0	0	0
10	1	0	1	0	0	0	0	0	0
11	1	0	1	1	0	0	0	0	0
12	1	1	0	0	0	0	0	0	0
13	1	1	0	1	0	0	0	0	0
14	1	1	1	0	0	0	0	0	0
15	1	1	1	1	0	0	0	0	0

Student Names: Elif Güler, Samed Düzçay  
Student IDs: 2015400099, 2015400027  
Group ID: 5

#### Experiment 4 (Analysis of a Sequential Circuit)

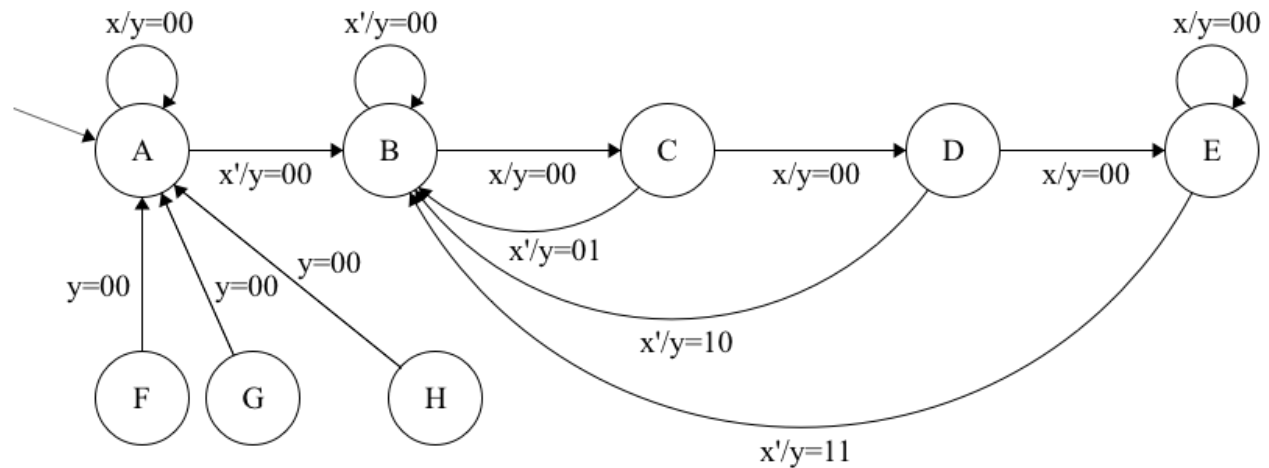**Step 5: Draw the finite state machine by using the truth table.**



(Mealy FSM with state encoding A: 000 – B: 001 – C: 010 - ... - H: 111)

**Step 6: How many unreachable states does the finite state machine contain? (No explanation, only short answer)**

# of Unreachable States: 3

**Step 7: Briefly explain the relation between the input and the output.**

Explanation: It's a sequence detector that:

- Ignores the initial 1's.
- Gives output  $y=01$  on input sequence 010.
- Gives output  $y=10$  on input sequence 0110.
- Gives output  $y=11$  on input sequence 011...10 (3 or more 1's).
- Detects overlapping input sequences such as 01010 (gives output  $y=01$  twice for this case).
- Gives output  $y=00$  otherwise.